

# POWER ELECTRONICS REFERENCE

CREATED BY KATHERINE A. KIM

JUNE 2010

## CONTENTS

1. Buck Converter	2
2. Boost Converter	3
3. Buck-Boost Converter	4

Page numbers reference *Elements of Power Electronics* by Philip T. Krein.

## 1. BUCK CONVERTER

Continuous Conduction Mode [p.123]

$$D_1 + D_2 = 1 \quad D_1 = \frac{V_{out}}{V_{in}}$$

$$V_{out} = D_1 V_{in} \quad I_{in} = D_1 I_{out}$$

$$I_{in} = D_1 I_L \quad I_{out} = I_L$$

Critical Conduction Mode


$$\Delta i_L = 2I_{out} \quad \Delta v_C = 2V_{out}$$

$$L_{crit} = \frac{(V_{in} - V_{out})D_1 T}{2I_{out}} \quad C_{crit} = \frac{I_{ripple} T}{16V_{out}}$$

Discontinuous Conduction Mode [p.330]

$$D_1 + D_2 + D_0 = 1 \quad D_1 V_{in} = (D_1 + D_2)V_{out}$$
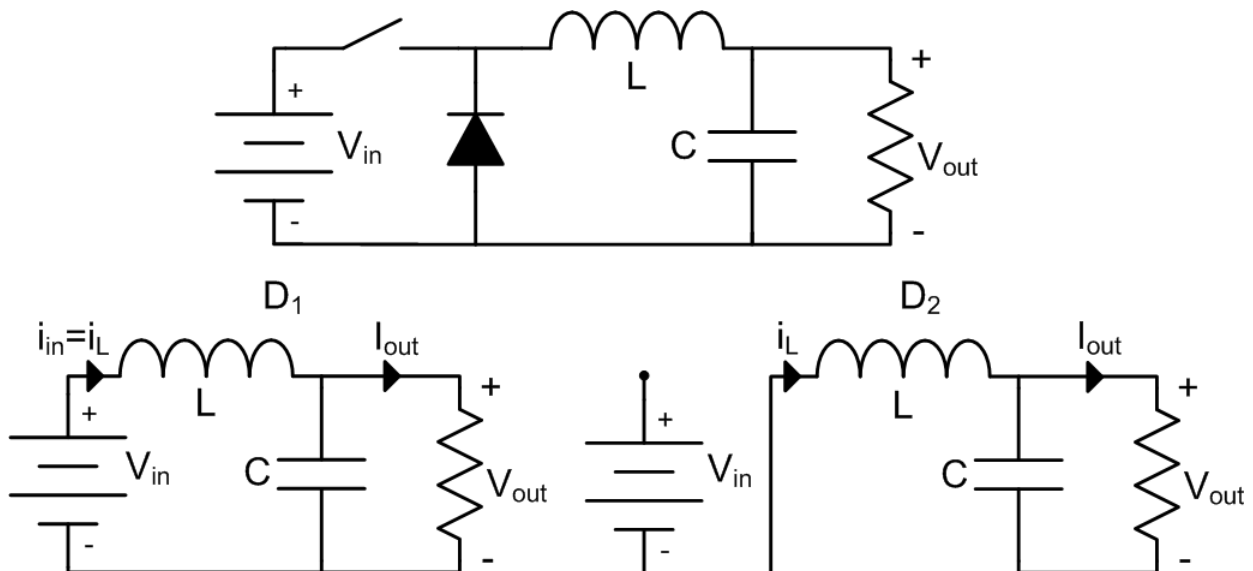
$$V_{out} = \frac{-D_1^2 V_{in} R T}{4L} + D_1 V_{in} \sqrt{\frac{R T}{2L} + \frac{R^2 T^2 D_1^2}{16L^2}} \quad I_{in} = (V_{in} - V_{out}) \frac{D_1^2 T}{2L}$$



## 2. BOOST CONVERTER

Continuous Conduction Mode [p.129]

$$D_1 + D_2 = 1 \quad D_1 = \frac{V_{out} - V_{in}}{V_{out}}$$

$$V_{out} = \frac{1}{1 - D_1} V_{in} \quad I_{in} = \frac{1}{1 - D_1} I_{out}$$

$$I_{in} = I_L \quad I_{out} = I_L D_2$$

Critical Conduction Mode


$$\Delta i_L = 2I_{in} \quad \Delta v_C = 2V_{out}$$

$$L_{crit} = \frac{V_{in} D_1 T}{2I_{in}} \quad C_{crit} = \frac{I_{out} D_1 T}{2V_{out}}$$

Discontinuous Conduction Mode [p.330]

$$D_1 + D_2 + D_0 = 1 \quad (D_1 + D_2)V_{in} = D_2 V_{out}$$
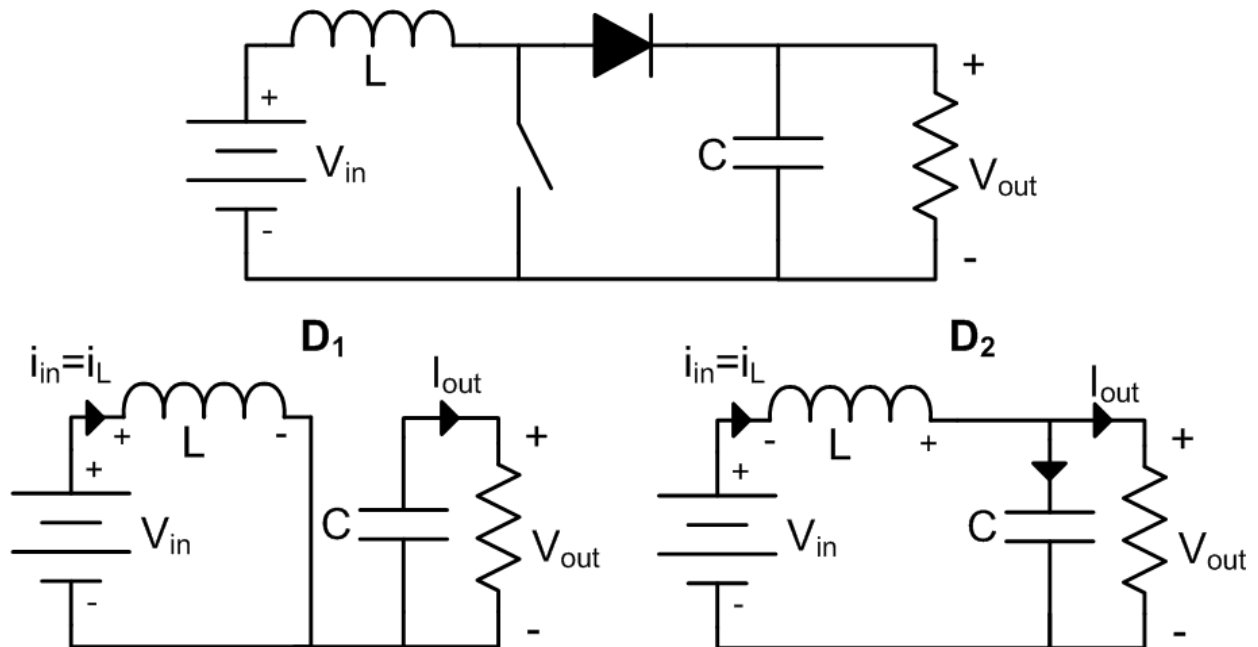
$$V_{out} = \frac{V_{in}}{2} + \frac{V_{in}}{2} \sqrt{1 + \frac{2D_1^2 RT}{L}} \quad I_{in} = (D_1 + D_2) \frac{V_{in} D_1 T}{2L}$$



## 3. BUCK-BOOST CONVERTER

(Polarity Reversal)

Continuous Conduction Mode [p.132]

$$\begin{aligned}
 D_1 + D_2 &= 1 & D_1 &= \frac{V_{out}}{V_{in} + V_{out}} \\
 V_{out} &= \frac{D_1}{1 - D_1} V_{in} & I_{in} &= \frac{D_1}{1 - D_1} I_{out} \\
 I_{in} &= D_1 I_L & I_{out} &= D_2 I_L \\
 I_{in} + I_{out} &= I_L & D_1 I_{out} &= D_2 I_{in}
 \end{aligned}$$

Critical Conduction Mode

$$\begin{aligned}
 \Delta i_L &= 2I_{out} & \Delta v_C &= 2V_{out} \\
 L_{crit} &= \frac{V_{in} D_1 T}{2I_{out}} & C_{crit} &= \frac{I_{out} D_1 T}{2V_{out}}
 \end{aligned}$$

Discontinuous Conduction Mode [p.330]

$$\begin{aligned}
 D_1 + D_2 + D_0 &= 1 & (D_1 + D_2)V_{in} &= D_2 V_{out} \\
 V_{out} &= \frac{V_{in}}{2} + \frac{V_{in}}{2} \sqrt{1 + \frac{2D_1^2 RT}{L}} & I_{in} &= (D_1 + D_2) \frac{V_{in} D_1 T}{2L}
 \end{aligned}$$

